

## EXPERIMENT 9

### REALIZATION OF LOGIC GATES USING VERILOG

#### Aim:

- 1) To write the Verilog HDL code for the following logic gates using dataflow modelling and simulate it in ModelSim.
  - a) NOT gate
  - b) AND gate
  - c) OR gate
  - d) XOR gate
  - e) NAND gate
- 2) To write the Verilog HDL code for the given Boolean function using dataflow modelling and simulate it in ModelSim.

$$F = A'B'C + ABC' + A'BC' + ABC$$

**CODE:** *(ON RIGHT SIDE)*

**DESIGN BLOCK:**

<>

**TEST BENCH:**

<>


#### Result:

- 1) The Verilog HDL code for the given logic gates is simulated in ModelSim and the output is obtained and verified.
- 2) The Verilog HDL code for the given Boolean function is simulated in ModelSim and the output is obtained and verified.


**NB: Diagram, Truth table and Screenshots of output: (on left side)**

**NB: Change the letter notation according to your program**


#### NOT gate:

 


#### AND gate

 


## OR gate

 

$$F = A'B'C + ABC' + A'BC' + ABC$$

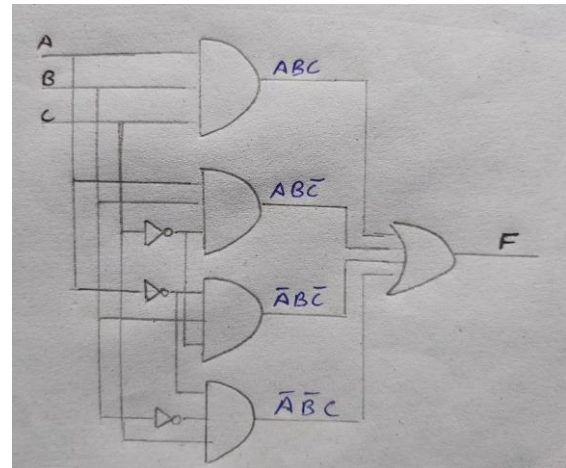


## XOR gate

 

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

## NAND gate

 

## EXPERIMENT 10

# REALIZATION OF ADDER AND SUBTRACTOR CIRCUITS USING VERILOG

### Aim:

- 1) Design Half adder, Full Adder, Half Subtractor, Full Subtractor circuits. Write the Verilog codes for the circuits and simulate them in ModelSim.
- 2) Write the Verilog code of Full Adder using Half Adder by using structural style of modelling and implement it in ModelSim.

**CODE:** (ON RIGHT SIDE)

**DESIGN BLOCK:**

<>

**TEST BENCH:**

<>


### Result:

- 1) The Verilog HDL code for Half adder, Full Adder, Half Subtractor, Full Subtractor circuits are simulated in ModelSim and the output is obtained and verified.
- 2) The Verilog HDL code for Full Adder using Half Adder by using structural style of modelling is simulated in ModelSim and the output is obtained and verified.

**NB: Diagram, Truth table and Screenshots of output: (on left side)**


**NB: Change the letter notation according to your program**

### HALF ADDER:

 


A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

### FULL ADDER

 


Cin	B	A	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

## HALF SUBTRACTOR

 


A	B	D	B <sub>0</sub>
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

## FULL SUBTRACTOR

 

A	B	C	D	Borrow
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1
 
## FULL ADDER USING HALF ADDER BY USING STRUCTURAL STYLE OF MODELING



A	B	C <sub>in</sub>	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

## EXPERIMENT 11

### REALIZATION OF 4:1 MULTIPLEXER AND 1:4 DEMULTIPLEXER CIRCUITS USING VERILOG

#### Aim:

- 1) Design a 4:1 Multiplexer circuit. Write the Verilog codes for the circuits and simulate them in ModelSim.
- 2) Design a 1:4 Demultiplexer circuit. Write the Verilog codes for the circuits and simulate them in ModelSim.

**CODE:** (ON RIGHT SIDE)

#### DESIGN BLOCK:

<>

#### TEST BENCH:

<>


#### Result:


- 1) The Verilog 4:1 Multiplexer circuit is simulated in ModelSim and the output is obtained and verified.
- 2) The Verilog 1:4 Demultiplexer circuit is simulated in ModelSim and the output is obtained and verified.

**NB: Diagram, Truth table and Screenshots of output: (on left side)**


**NB: Change the letter notation according to your program**

#### 4:1 MULTIPLEXER:

 


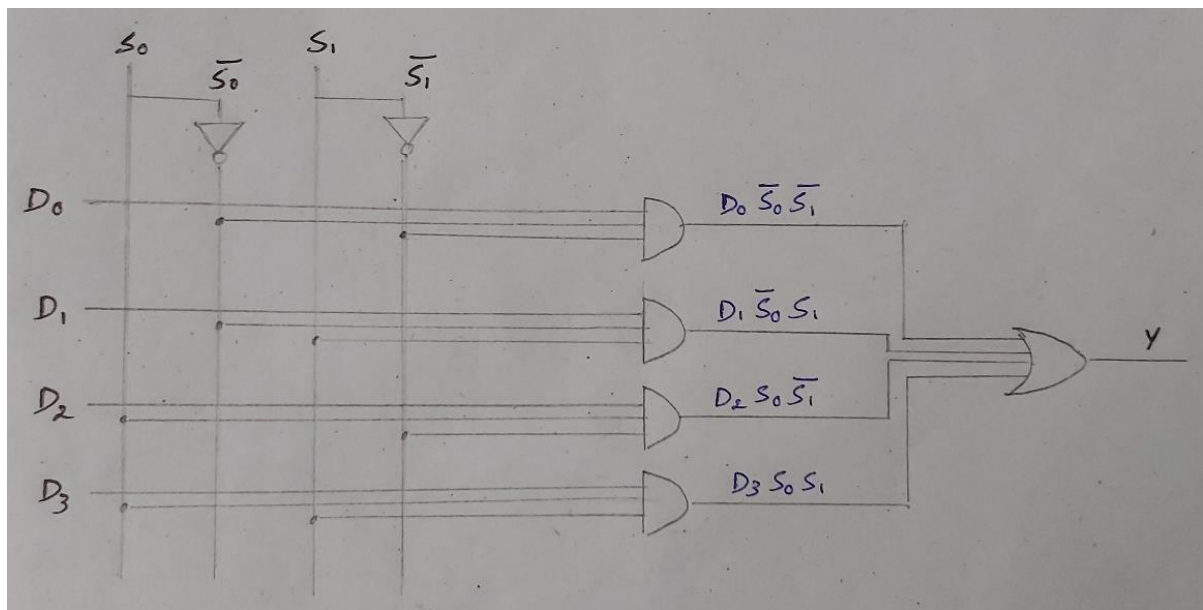

### 1:4 DEMULTIPLEXER

 



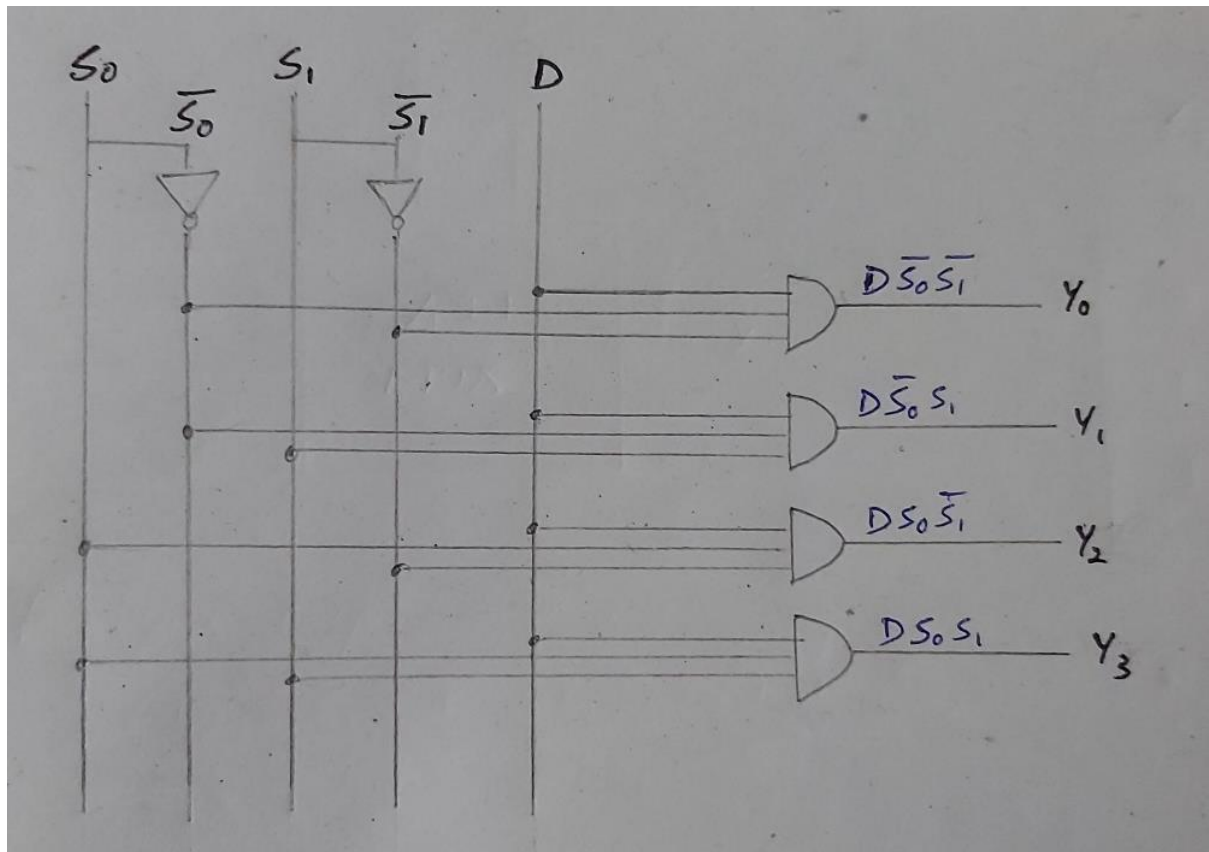

## EXPERIMENT 12

# REALIZATION OF D, T, SR, JK FLIP FLOPS AND 4-BIT UP COUNTER USING STRUCTURAL STYLE OF MODELING USING VERILOG

### Aim:

- 1) Design and implement the Verilog code of D, T, SR & JK flip flops and stimulate them in ModelSim.
- 2) Design and implement the Verilog code for 4-bit up counter using structural style of modelling and simulate it in ModelSim.

**CODE:** (*ON RIGHT SIDE*)

### DESIGN BLOCK:

<>

### TEST BENCH:

<>


### Result:

- 1) The Verilog HDL code for the given logic gates is simulated in ModelSim and the output is obtained and verified.
- 2) The Verilog HDL code for the given Boolean function is simulated in ModelSim and the output is obtained and verified.

**NB: Diagram, Truth table and Screenshots of output: (on left side)**


**NB: Change the letter notation according to your program**

### D FLIP FLOP:

 





## T FLIP FLOP

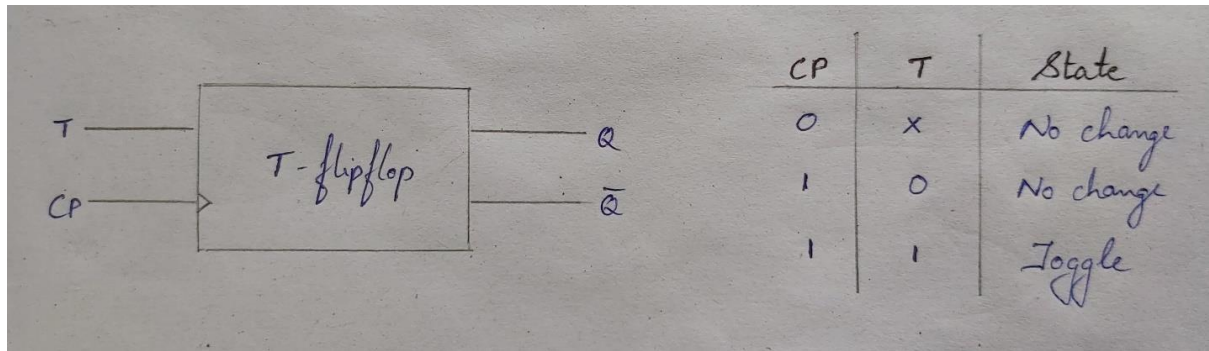

## SR FLIP FLOP

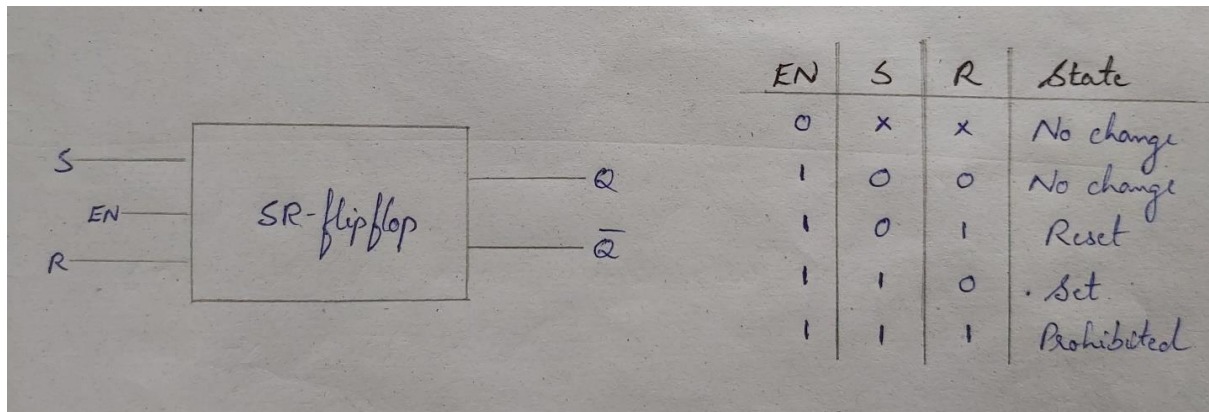

## JK FLIP FLOP

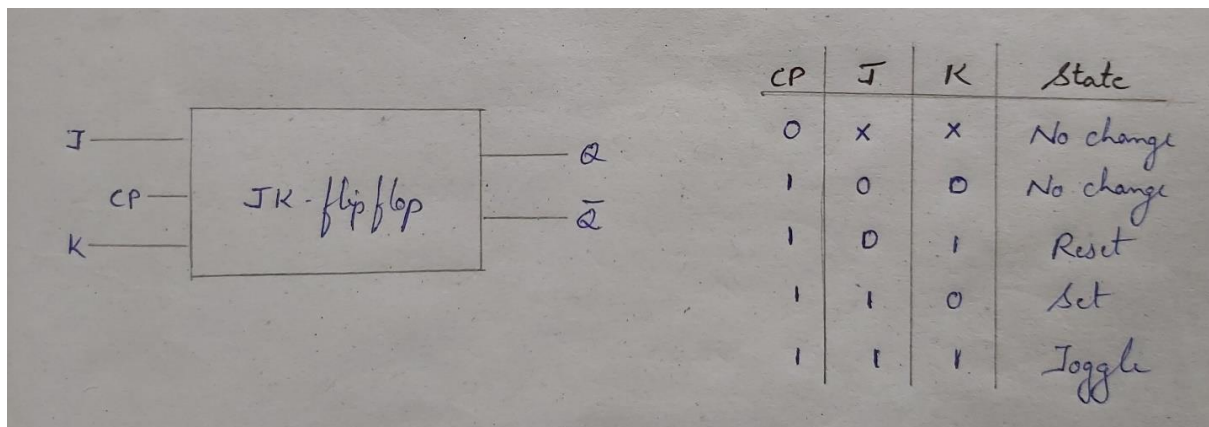

## 4-BIT UP COUNTER USING STRUCTURAL STYLE OF MODELING

